

Lab Division Algorithm

Kinner Parikh

October 16, 2022

CMPEN 331 - 001

1 Code

```
'timescale 1ns / 1ps
module src(
    input clk, clrn, start, [31:0] a, [15:0] b,
    output reg [15:0] reg_r, reg [31:0] reg_q, reg [4:0] count, reg busy, re
);
    reg [15:0] reg_b;

    wire [16:0] sub_out;
    wire [16:0] subtrahend = {1'b0, reg_b};
    wire [16:0] minuend = {reg_r, reg_q[31]};
    sub sub_mod(minuend, subtrahend, sub_out);

    wire [15:0] r = {reg_r[14:0], reg_q[31]};
    wire sub_mux_sel = sub_out[16];
    wire [15:0] sub_mux_out;
    sub_mux sub_mux_mod(r, sub_out[15:0], sub_mux_sel, sub_mux_out);

    wire [31:0] ina = a;
    wire [31:0] q = {reg_q[30:0], !sub_out[16]};
    wire [31:0] q_mux_out;
    q_mux q_mux_mod(ina, q, start, q_mux_out);

    always @(posedge clk)
    begin
        //innebeneningin
        if (clrn == 0)
        begin
            reg_b <= 0;
            reg_q <= 0;
            reg_r <= 0;
            count <= 0;
            ready <= 0;
            busy <= 0;
        end
        else if (start == 1)
        begin
            reg_b <= b;
            reg_q <= q_mux_out;
            reg_r <= 0;
            count <= 0;
        end
    end
endmodule
```

```

        ready <= 0;
        busy  <= 1;
    end
    else if (busy == 1)
    begin
        reg_q <= q_mux_out;
        reg_r <= sub_mux_out;
        count <= count + 1;
        if (count == 31)
        begin
            busy <= 0;
            ready <= 1;
        end
    end
end
end
endmodule

```

```
'timescale 1ns / 1ps
module sub(minuend, subtrahend, difference);
    input [16:0] minuend;
    input [16:0] subtrahend;
    output reg [16:0] difference;

    always @(*)
    begin
        difference = minuend - subtrahend;
    end
endmodule
```

```

`timescale 1ns / 1ps
module sub_mux(r, sub_in, sel, reg_r);
    input [15:0] r;
    input [15:0] sub_in;
    input sel;
    output reg [15:0] reg_r;

    always @(*)
    begin
        if (sel == 1) // negative case
        begin
            reg_r = r;
        end
        else // positive case
        begin
            reg_r = sub_in[15:0];
        end
    end
endmodule

```

```

`timescale 1ns / 1ps

module testbench();
    reg clrn, start, clk;
    reg [31:0] a;
    reg [15:0] b;
    wire [31:0] q;
    wire [15:0] r;
    wire busy, ready;
    wire [4:0] count;


    src div(clk, clrn, start, a, b, r, q, count, busy, ready);
    initial
    begin
        clrn = 0;
        start = 0;
        clk = 1;
        a = 'h4c7f228a;
        b = 'h6a0e;
        #5
        start = 1;
        clrn = 1;
        #10
        start = 0;


        #325
        clrn = 0;
        start = 0;
        a = 'hffff00;
        b = 'h4;
        #5
        start = 1;
        clrn = 1;
        #10
        start = 0;
    end
    always
    begin
        #5
        clk = ~clk;
    end
endmodule

```


2 Images

Timing Waveform

 

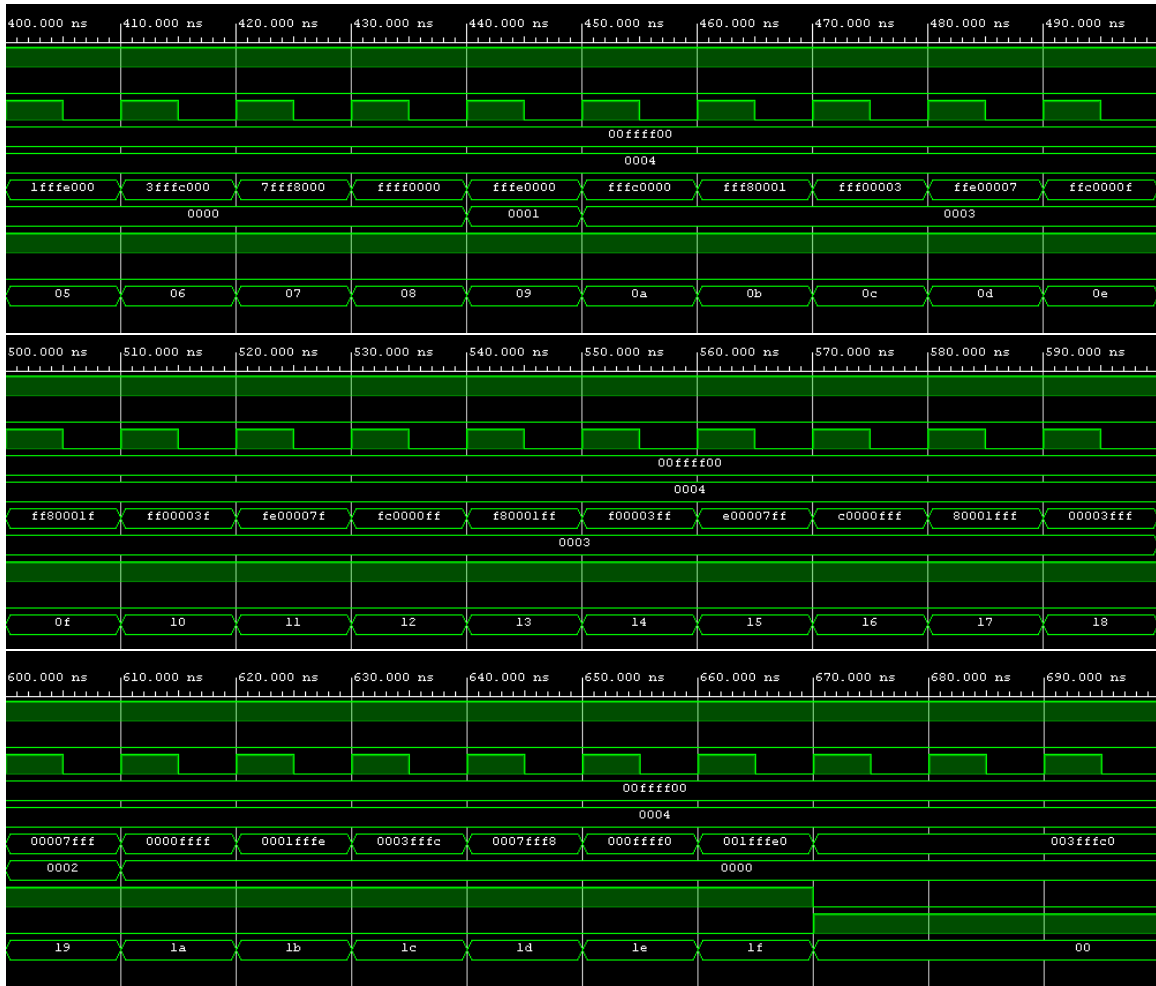

Schematic

 

I/O Planning

